

ST. JOSEPH'S COLLEGE (AUTONOMOUS), BANGALORE-27  
B.Sc. PHYSICS -V SEMESTER  
SEMESTER EXAMINATION-OCTOBER 2019  
**PH 5115: ELECTRONICS AND RELATIVITY.**

**Time: 2½ hours**

**Max.Marks:70**

This question paper has **two** printed pages and **three** parts

**PART-A**

Answer any **Four** of following: (4x10=40)

1. a) With the circuit diagram explain the action of transistor( CE) as an amplifier. (8+2)  
b) Define  $\alpha$  and  $\beta$  of a transistor.
2. a) Explain the construction of JFET. (2+8)  
b) With a circuit diagram explain the drain and transfer characteristics of JFET.
3. a) Explain the working of phase shift oscillator with a circuit diagram and discuss the condition for frequency of oscillation. (5+5)  
b) Give the construction and working of differentiator circuit using operational amplifier.
4. a) What is a logic gate? Explain the construction and working of AND, OR gates using diodes. Give the truth table of them. (7+3)  
b) State and prove De-Morgan's theorem.
5. a) Define proper length and proper time. Derive an expression for length contraction. (7+3)  
b) State the postulates of special theory of relativity.
6. Describe Michelson-Morley experiment and discuss the negative result. (10)

**PART-B**

Solve any **Four** of the following: (4x5=20)

7. A transistor is connected in CE configuration. Draw the d.c.load line and determine the operating point .Given:  $V_{cc} = 12V, R_c = 6 \text{ k}\Omega, I_B = 20 \mu A, \beta = 50$ .
8. In a Hartley Oscillator  $L_1 = 0.2\text{mH}$ ,  $L_2 = 20\mu\text{H}$  and  $M = 40\mu\text{H}$ . Find the value of capacitor of the oscillatory circuit to obtain a frequency of 4.1MHz.
9. A JFET has  $I_D$  of 5mA. If the shorted gate drain current is  $I_{DSS} = 10\text{mA}$  and  $V_{GS(\text{off})} = -6V$ . Find the values of  $V_{GS}$  and  $V_P$ .

10. An atomic particle has a rest mass of  $3 \times 10^{-25}$  kg. Find its total energy when (i) It is at rest and (ii) It has a velocity of  $0.8c$ .
11. Calculate the velocity of an elementary particle, whose mass is 10 times its rest mass.
12. In an inverting amplifier if  $R_i = 10\text{k}\Omega$ ,  $R_f = 100\text{k}\Omega$  and the supply voltages are  $\pm 18\text{V}$ , find (i) closed loop voltage gain (ii) Input impedance (iii) Maximum operating frequency.  
Given:  $V_{in} = 1\text{ V}_{pp}$ , the slew rate  $= 0.5\text{V}/\mu\text{s}$

### PART-C

Answer any **Five** of the following:

(5x2=10)

13. (a)  $\alpha$  of a transistor is unity still it is called as current gain. Why?
- (b) What is the basic condition for the proper functioning of a transistor as an amplifier?
- (c) Even though the gain in open loop condition of an op amp is quite large, but it is seldom used. Why?
- (d) Which gate is called universal gate? Justify.
- (e) Why the ideas of relativity seems to be strange in day to day life? Explain.
- (f) If momentum is conserved in a collision of two as measured on a uniformly moving train, is it also conserved for the ground observer? Explain.